

HOMEWORK : 02
K.SURYA PRAKASH
EE18BTECH11026

Question : 01

1. Transient simulations for NMOS and PMOS, to find the R_{eq} (L = 0.18um process)

$$R_{eq} \sim (R_{Vdd} + R_{Vdd/2})/2$$

1.1 NMOS : For Vdd = 1.8V

```
*** For Ques: 1. NMOS
*** Vgs = 1.8V, init Vds = 1.8V.,

** M1 --> 1. W/L = 240/180
** M2 --> 2. W/L = 400/180

.include TSMC180.lib
.model nch_tt nmos (level = 8)


Vgs  g      0      1.8
V_am d      am     0V    ** ammeter
C     am     0      1e-12    IC = 1.8V
*M1   d      g      0      0 nch_tt W=240n L = 180n
M2    d      g      0      0 nch_tt W=400n L = 180n

.ic V(am) = 1.8V
.control

tran 1p 13n
*plot V(am)
*plot -i(V_am) vs V(am) title "I vs V"
plot V(am)/-i(V_am) vs V(am) title "Res vs V: M1 "
wrdata 1.a.n.2.dat V(am) V(am)/-i(V_am)
```


```
.endc  
.end
```

1.1.1 $W/L = 240/180$

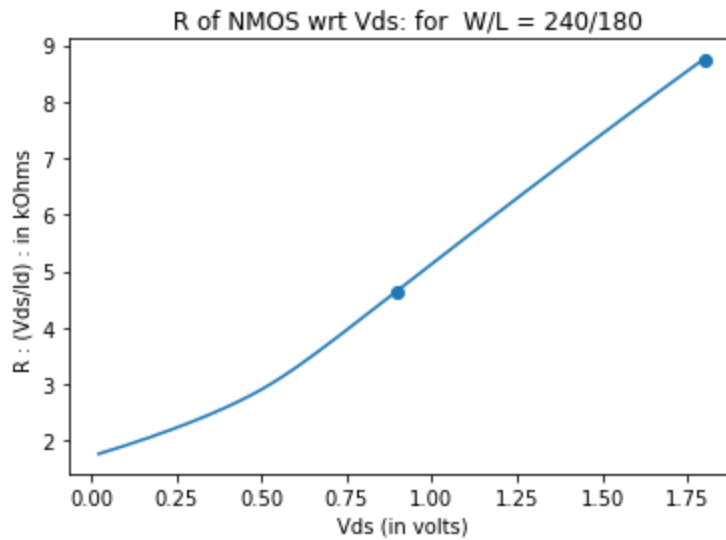

Calculating $R_{eq} = (8.8 + 4.7)/2 = \mathbf{6.75 \text{ kOhm}}$

1.1.2 $W/L = 400/180$

 

Calculating $R_{eq} = (6.2 + 3.36)/2 = \mathbf{4.78 \text{ kOhm}}$

1.2 : PMOS : for $V_{dd} = -1.8V$

```
*** For Ques: 1. PMOS
*** Vgs = -1.8V, init Vds = -1.8V.,
** M1 --> 1. W/L = 240/180
** M2 --> 2. W/L = 400/180

.include TSMC180.lib
.model pch_tt pmos (level = 8)

Vgs  g    0    -1.8
V_am d    am   0    ** ammeter
C     am   0    1e-12    IC = -1.8V
*M1   d    g    0    0 pch_tt W=240n L = 180n
M2    d    g    0    0 pch_tt W=400n L = 180n


.ic V(am) = -1.8V

.control

tran .5p 30n
*plot -V(am)
*plot -i(V_am) vs V(am) title "I vs V"
plot V(am)/-i(V_am) vs V(am) title "Res vs V: M1 "
wrdata 1.a.p.2.dat V(am) V(am)/-i(V_am)


.endc
.end
```

1.2.1 $W/L = 240/180$

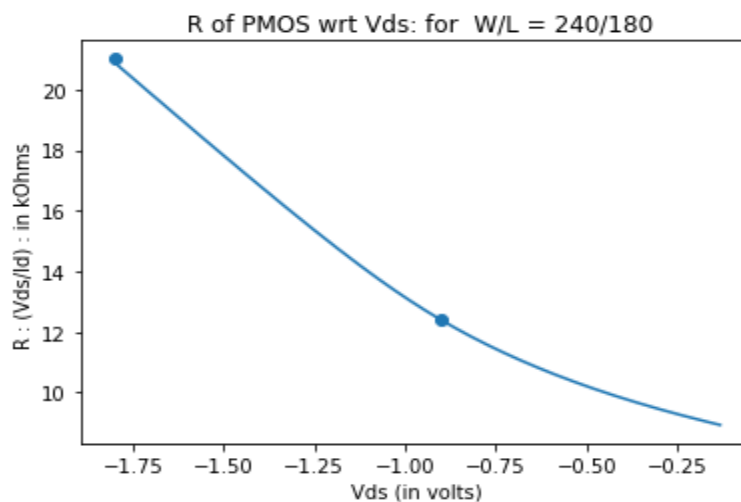

Calculating $R_{eq} = (21 + 12.4)/2 = 16.7 \text{ k}\Omega$

1.2.2 : $W/L = 400/180$

 

Calculating $R_{eq} = (15.2 + 8.9)/2 = 12.05 \text{ k}\Omega$

b) Results for different Vdd : Trend of R_{eq} w.r.t V_{dd}

By doing analysis for different V_{dd} : (initial capacitor voltage and V_{gs}). The below are the results for R_{eq} at different Vdd.

For $W/L : 240/180$

Vdd (in V)	Req for NMOS (k Ohm)	Req for PMOS(k Ohm)
1.8	6.75	16.7
1.5	7.53	21.8

1.2	9.3	32.6
0.9	14.47	62.5
0.6	63.5	251

For W/L : 400/180 :

Vdd (in V)	Req for NMOS (k Ohm)	Req for PMOS(k Ohm)
1.8	4.78	12.05
1.5	5.375	15.25
1.2	6.75	22.1
0.9	10.55	40.65
0.6	51.3	193.7

Observations :

1. We can see that there is a deviation with the values mentioned in the Textbook , where results are produced for (W/L = 1).
2. R_{eq} is inversely proportional to (W/L) ratio.
3. We can observe that when we scale the obtained R_{eq} with (W/L) we get the values closer to that of the TB values.

4. Although there will be differences, since the simulation is done for a 0.25u process (in the TB), while we performed for a 0.18u process
 5. Another observation is that R_{eq} of PMOS is relatively high when compared to that of NMOS for the same V_{dd} , reason being that since PMOS works with the mobility of holes which is less when compared to the mobility of electrons in NMOS. This will result in less current, which is seen as a high resistance in PMOS devices.
 6. R_{eq} decreases as V_{dd} increases, and reaches a constant low value for high V_{dd} . As V_{dd} increases, the mosfet moves from : Cutoff to saturation region. At cutoff very less current flows, and seen as high resistance. And for high V_{dd} , it reaches saturation, where current is constant and high and does not depend on V_{gs} . This is seen as a low ON resistance.
-

Question : 02

MOSFET Capacitance

$$V_{app} = V_{CM} + (1/(2\pi f)) \sin(\omega t)$$

$$I_g = C \cos(\omega t)$$

The amplitude of the gate current gives the gate capacitance.

A. CV CHARACTERISTICS :

```
*** For Ques: 2 NMOS
*** Vgs = Vcm + sin(wt), Vds = 0V., sweeping vcm

** M1 --> 1. long channel
** M2 --> 2. short channel

.include TSMC180.lib
.model nch_tt nmos (level = 8)
.param f= 10e6
*.param f = 10e9
Vgs  g      a      dc 0 SIN(0 {1/(2*3.14*f)} f 0 0 0 )
Vcm  a      0      -2V
*MI   0      g      0      0      nch_tt W=25u L = 10u
Ms   0      g      0      0      nch_tt W = 450n L=180n

.control
let v = -2
let v_vec = vector(20)
let c_vec = vector(20)
let loop = 0
while v <1.8
    alter @Vcm v

    tran 1n 1u
    *tran .1p 10n

    meas tran i_max FIND i(Vcm) AT = 1u
    *meas tran i_max FIND i(Vcm) AT = 10n

print v
*plot i(Vcm) xlabel "Current at Vcm = $&v"

let v_vec[loop] = v
let c_vec[loop] = -i_max
```

```

let v = v + 0.2
let loop = loop + 1

end


plot c_vec vs v_vec
wdata 2.b.dat c_vec vs v_vec
.endc
.end

```


Generating C vs V_{cm} graph.

Frequency : 10MHz

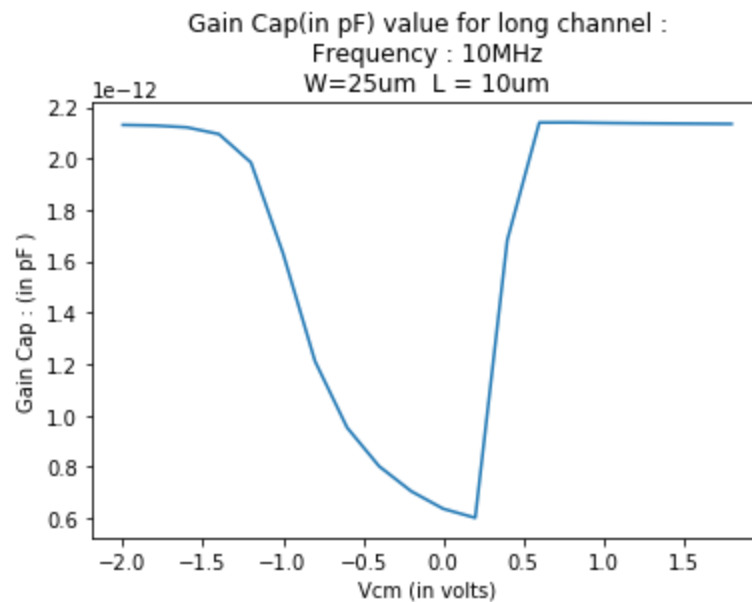A.1. $W/L = 2.5$; Long channel $L = 10\mu m$, $W = 25\mu m$.



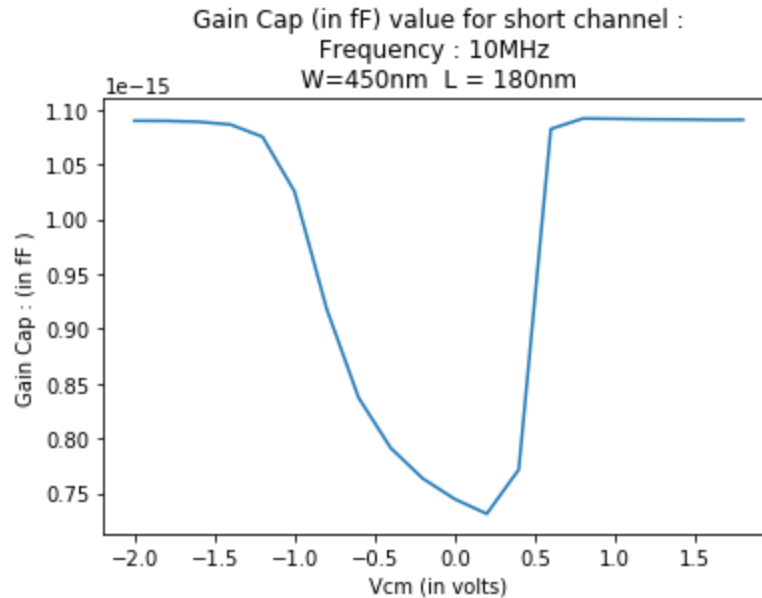A.2. Short channel : $L = 180nm$, $W = 450nm$



OBSERVATIONS

1. Long channel capacitance (pF) is higher than short channel capacitance (fF).
2. The highest value depends on $C_{OX} * W * L$. Hence it is evident that long channels have a higher cap in order than short channels.
3. The overlap capacitance comes into picture in the short channel case (since it's very small).

Explaining the graph :



3.1 Cutoff : The Gate-Bulk cap (C_{GBS}) accounts for the left side of the graph ($< 0V$), which gradually reduces as V_{cm} (i.e; V_{gs}) increases, due to the formation of channel

3.2 Linear : A complete channel is formed , later on the capacitance is provided by the source and the drain equally and C_{GBS} ceases to exist.

B) Low vs High Frequency :

Plots for 10MHz are shown above.

Plots for 10 GHz

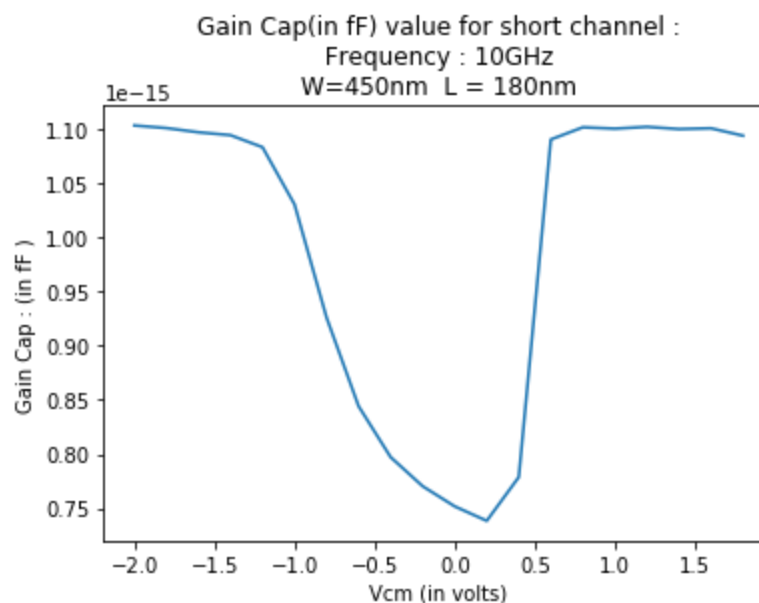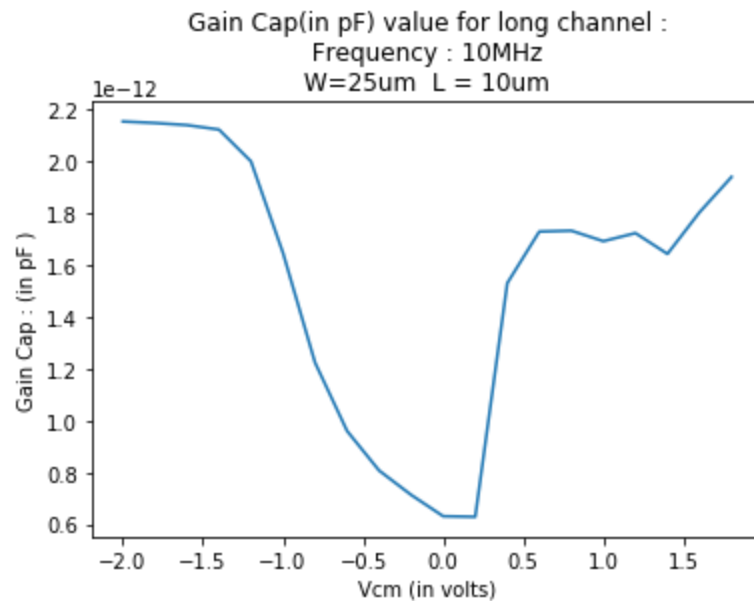

Observations :

1. We can see that both plots are almost identical with a similar range.
 2. Long channel continuous to be in pF range, and short channel in fF range. (due to its dependence on $W \cdot L$).
 3. Due to abundant charges provided by source and the drain , we are able to find similar plots at different frequencies , unlike a MOSCAP, which shows different characteristics due to absence of drain and source.
-

Question : 03

3Q)

$$V_{TN} = |V_{TP}| = 0.3V$$

$$V_{DD} = 1.2V$$

a) which one consumes static power?
at high input?

→ $(i), (ii), (iii)$

CMOS (iv) has no current flow
due to presence of a PMOS (at OFF
state)

Another case, since NMOS is ON
current flows \Rightarrow static power consumed

b) Static power at low input?

→ $\boxed{\text{None}}$

→ No current is drawn, since ~~PMOS~~
NMOS are off state in every case

(c) $V_{OH} = 1.2V$?

$(i) \quad (ii) \quad (iv)$

\Rightarrow (i) MOS is off \Rightarrow no current

$$\Rightarrow \boxed{V_{out} = 1.2V} \quad \checkmark$$

\Rightarrow (ii) NMOS at bottom requires

no current $\Rightarrow V_{GS} - V_T = 0$ (of top NMOS)

$$\Rightarrow \boxed{V_{out} = 0.9V} \quad \times$$

\Rightarrow (iii) No current at bottom

$$V_{GS} = V_T = 0V$$

$$\Rightarrow \boxed{V_S = V_{out} = 1.2V} \quad \checkmark$$

\Rightarrow (iv) NMOS is open \Rightarrow

no current is allowed

$$\Rightarrow \boxed{V_{out} = 1.2V} \quad \checkmark$$

(d) $V_{OL} = 0V$?

(iV)

Reason: Since both

For i, ii, iii \Rightarrow current is drawn.

\Rightarrow ~~to~~ V_{out} is found by voltage divider network. \Rightarrow Hence $V_{out} \neq 0$

For CMOS:

PMOS is open $\Rightarrow V_{out} = 0$

(e) (i) (ii) (iii)

All except CMOS are dependent on size of devices

Question 04

Q4) NMOS inverter.

a) $V_{OH} \Rightarrow$ Since $V_{IN} = 0V$
 \Rightarrow No major current \Rightarrow ~~Major drop~~ across R_L

~~0~~

$$\Rightarrow \boxed{V_{out} = 2.5V} \Rightarrow V_{OH}$$

* V_{OL} :- $V_{IN} = 2.5V (V_{DD})$

* Here NMOS in linear region.

$$\frac{K'_L}{L} \left((V_{GS} - V_T) V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{V_{DD} - V_{OL}}{R_L}$$

$$\Rightarrow K'_L = 345 \times 10^{-6}$$


$$\Rightarrow (345 \times 10^{-6}) (75 \times 10^{-3}) \left(2.07 V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{2.5 - V_{OL}}{R_L}$$

$$\Rightarrow (25.87) \left(2.07 V_{OL} - \frac{V_{OL}^2}{2} \right) = 2.5 - V_{OL}$$

$$\rightarrow \boxed{V_{OL} = 46.33 \text{ mV}}$$

* V_M : $\therefore V_{in} = V_{out}$

 $\Rightarrow \frac{k'W}{2L}$ (NMOS in saturation)



$$\Rightarrow \frac{k'W}{2L} (V_M - V_T)^2 = \frac{V_{DD} - V_M}{R_L}$$

$$\Rightarrow 172.5 \times 10^6 (V_M - 0.43)^2 = \frac{2.5 - V_M}{75 \times 10^3}$$

$$\Rightarrow 12.9 (V_M - 0.43)^2 = 2.5 - V_M$$

\Rightarrow Solving the Quad eqn.

$$\boxed{V_M = 0.79 \text{ V}}$$

(b) * $V_{IL}, V_{IH} = ?$

$$\text{For } V_{IL}, V_{IH} \Rightarrow \frac{dV_{out}}{dV_{in}} = -1$$

① V_{IL} (NMOS is saturation region).

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{K'_N}{2L} (V_{in} - V_T)^2$$

\Rightarrow Derivating wrt. V_{in}

$$\Rightarrow \frac{-1}{R_L} \left(\underbrace{\frac{dV_{out}}{dV_{in}}}_{-1} \right) = \frac{K'_N}{2L} (2) (V_{in} - V_T)$$

$$\Rightarrow \frac{1}{R_L} = \frac{K'_N}{L} (V_{in} - V_T)$$

$$\Rightarrow \cancel{V_{in}} V_{IL} = V_{in} = \frac{L}{K'_N R_L} + V_T$$

$$= \frac{10^6}{(1035) \times (15 \times 10^3)} + 0.43$$

~~$V_{IL} = 0.468 V$~~

$V_{IL} = 0.468 V$

$$V_{IL} = 0.468V$$

* V_{IH} (NMOS in linear region)

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{K'_N W}{L} \left[(V_{IN} - V_T) V_{out} - \frac{V_{out}^2}{2} \right] \quad (1)$$

$$\rightarrow -\frac{1}{R_L} \frac{dV_{out}}{dV_{in}} = \frac{K'_N W}{L} \left[(V_{IN} - V_T) \frac{dV_{out}}{dV_{in}} + V_{out} - 2 \frac{V_{out}}{2} \frac{dV_{out}}{dV_{in}} \right]$$

$$\Rightarrow \frac{1}{R_L} = \frac{K'_N W}{L} [V_T - V_{in} + 2 \cdot V_{out}]$$

$$\Rightarrow \frac{L}{R_L K'_N W} = V_T - V_{in} + 2 V_{out}$$

$$\Rightarrow V_{in} = V_T + 2 \cdot V_{out} - \frac{L}{R_L K'_N W} \rightarrow (2)$$

\Rightarrow Solving (2), (1) =

$$\Rightarrow 2.5 - V_{out} = \frac{R_L K'_N W}{L} \left[\left(2V_{out} - \frac{L}{R_L K'_N W} \right) V_{out} - \frac{V_{out}^2}{2} \right]$$

on Solving this;

$$\boxed{V_{out} = } \rightarrow 0.253 \text{ V}$$

$$\Rightarrow V_{IH} = V_{in} = 2V_{out} + V_T \approx 0.012$$

$$\Rightarrow \boxed{V_{IH} = V_{in} = } \rightarrow 0.899 \text{ V}$$

B) contd.

Noise margin

$$N_{MH} = V_{OH} - V_{IH} = 2.5 - 0.9 \\ = 1.6 \text{ V}$$

$$N_{ML} = V_{IL} - V_{OL} \\ = 0.468 - 0.046 \\ = 0.42 \text{ V}$$

(c) Peak gain \Rightarrow happens at V_m
($V_{in} = V_{out}$) \Rightarrow Saturation sgn

$$\frac{k'W}{2L}(V_m - V_T)^2 = \frac{V_{DD} - V_{out}}{R_L}$$

$$\Rightarrow \left. \frac{\partial V_{out}}{\partial V_{in}} \right|_{V_{in}=V_m} \Rightarrow \text{gain}$$

$$\Rightarrow \frac{k'W}{2L}(2(V_m - V_T)) = \frac{-1}{R_L} \left(\frac{\partial V_{out}}{\partial V_{in}} \right)$$

$$\Rightarrow \frac{-R_L k'W}{L}(V_m - V_T) = \text{gain (peak)}$$

Solving

$$\text{Peakgain} : \Rightarrow 25.875 (0.793 - 0.43) \\ \rightarrow 9.38 \underline{\underline{V}}$$

$$\boxed{\text{Peakgain} = -9.38V}$$

Ques 5 : NMOS

5a) VTC plots :

```
** Q5. VTC of NMOS with res

.include TSMC180.lib
.model nch_tt nmos

M vout input 0 0 nch_tt W = 0.54u L = 0.18u
R vout vdd 75k
Vin input 0 dc
V Vdd 0 2.5V

.control
dc Vin 0 3 .01



plot V(vout) vs v(input)
plot deriv(V(vout))

let diff=deriv(V(vout))
let peakgain=deriv(diff)
meas dc vIL find V(input) when diff=-1 cross=1
meas dc vIH find V(input) when diff=-1 cross=2
meas dc vOH find V(vout) when V(input)=0 cross=1
meas dc vOL find V(vout) when V(input)=2.5 cross=1
meas dc vM find V(vout) when V(input)=V(vout) cross=1
meas dc gain_peak find diff when peakgain=0

wrdata 5.a.1.dat V(vout) vs v(input)
wrdata 5.a.2.dat deriv(V(vout)) vs v(input)

.endc
.end
```

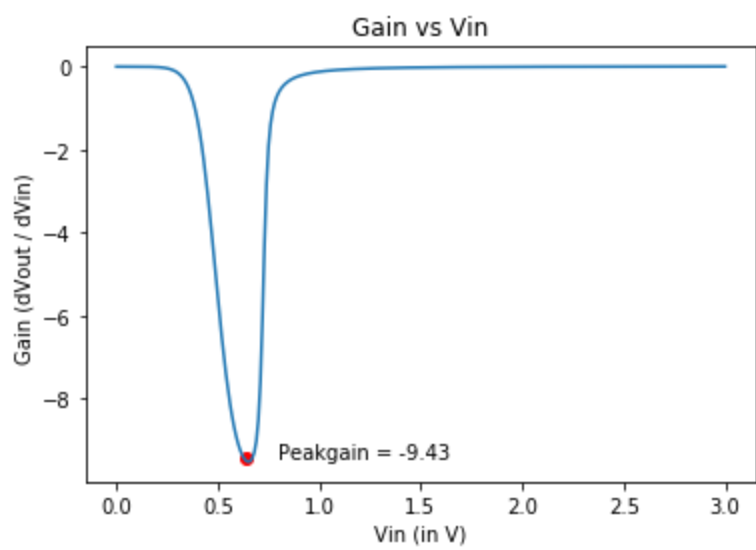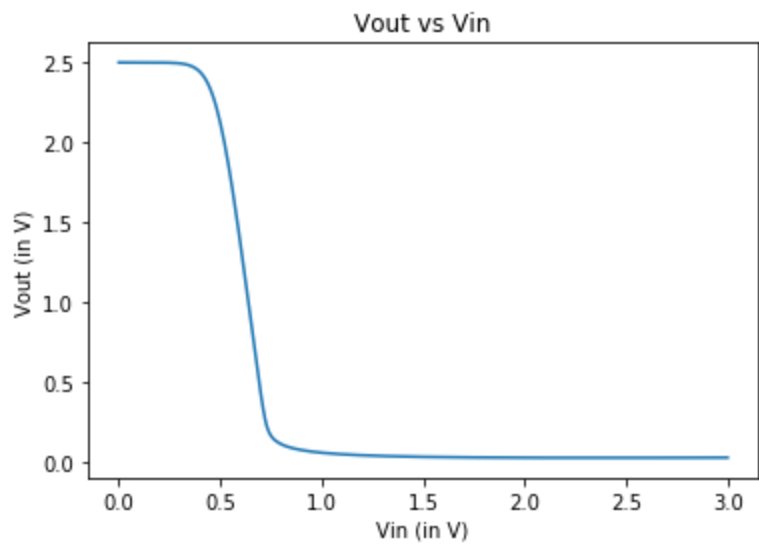**Plotting the gain (dV_{out}/dV_{in}) and V_{out} vs V_{in}
For $R_L = 75k$ Ohms**



Parameters	Observed Value
V_{IL}	0.387 V
V_{IH}	0.774 V
V_{OH}	2.49 V

V_{OL}	0.031 V
V_M	0.67 V
Peak gain	-9.43

5b) Change of threshold and peak gain w.r.t load resistance.



Varying resistance : checking for : 50k, 120k , 190k.

```
.include TSMC180.lib
.model nch_tt nmos

M vout input 0 0 nch_tt W=0.54u L=0.18u
R vout vdd 75k
Vin input 0 dc
V vdd 0 2.5V
.control
dc Vin 0V 3V 0.01V R 50k 200k 70k

plot V(vout)
plot deriv(V(vout))
let diff=deriv(V(vout))
let peakgain=deriv(diff)
meas dc vil find V(input) when diff=-1 cross=1
meas dc vih find V(input) when diff=-1 cross=2
meas dc voh find V(vout) when V(input)=0 cross=1
meas dc vol find V(vout) when V(input)=2.5 cross=1
meas dc vm find V(vout) when V(input)=V(vout) cross=1
meas dc gain_peak find diff when peakgain=0

  wrdata 5.b.1.dat V(vout) vs v(input)
wrdata 5.b.2.dat deriv(V(vout)) vs v(input)
.endc
.end
```



Observations :

1. As R_L increases, V_M decreases, this is a consequence of the Pull down network becoming stronger.
2. Also the peak gain increases by magnitude. This happens due to the movement of V_M towards V_{IL} , hence the slope needs to drop at a high rate, this in turn increases the peak gain.

5c.) Implementing an inverter : Testing with a square pulse of $f = 250\text{k Hz}$, $C_L = 3\text{pF}$.

```
.include TSMC180.lib
.model nch_tt nmos

M vout input 0 0 nch_tt W = 0.54u L = 0.18u
R vout vdd 75k

** input Vmax 1V, 50 per duty cycle , freq : 25kHz
Vin input 0 PULSE(0 2.5 0 0 0 2u 4u)
V Vdd 0 2.5V
C vout 0 3p

.tran 0.01u 10u 6u
.control
run
plot V(input)
plot V(vout)

meas tran vout(max) MAX V(vout)
meas tran input(max) MAX V(input)

let v_half = vout(max)/2
let v_10 = 0.1*vout(max)
let v_90 = 0.9*vout(max)
let vin_half = 1.25
meas tran tr_10 when V(vout) = v_10 cross = 1
meas tran tr_90 when V(vout) = v_90 cross = 1

meas tran tf_90 when V(vout) = v_90 cross = 2
meas tran tf_10 when V(vout) = v_10 cross = 2
meas tran tr_half_1 when V(vout) = v_half cross = 1
meas tran tr_half_2 when V(vout) = v_half cross = 2



meas tran tin_half1 when V(input) = vin_half cross = 1
meas tran tin_half2 when V(input) = vin_half cross = 2

let tpl = tr_half_1 - tin_half1
let tph = tr_half_2 - tin_half2
let tp =(tpl+tph)/2

let tr = tr_90 - tr_10
let tf = tf_10 - tf_90
```

```
print tr tf
print tpl tph
print tp

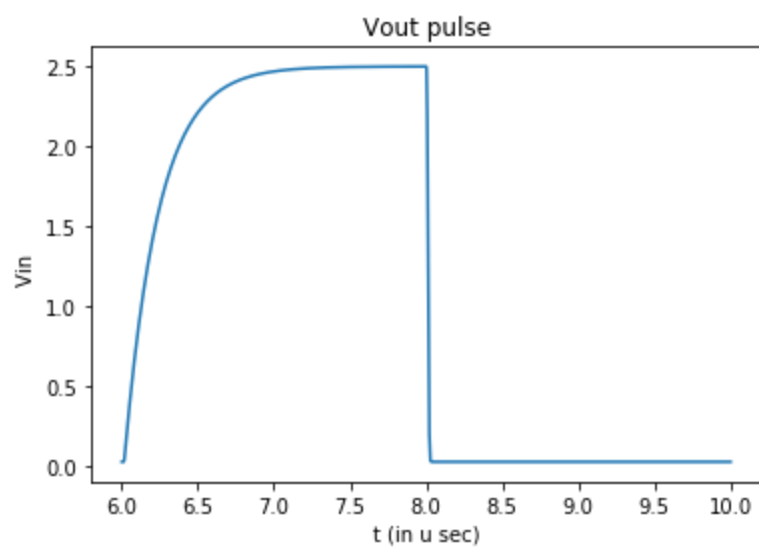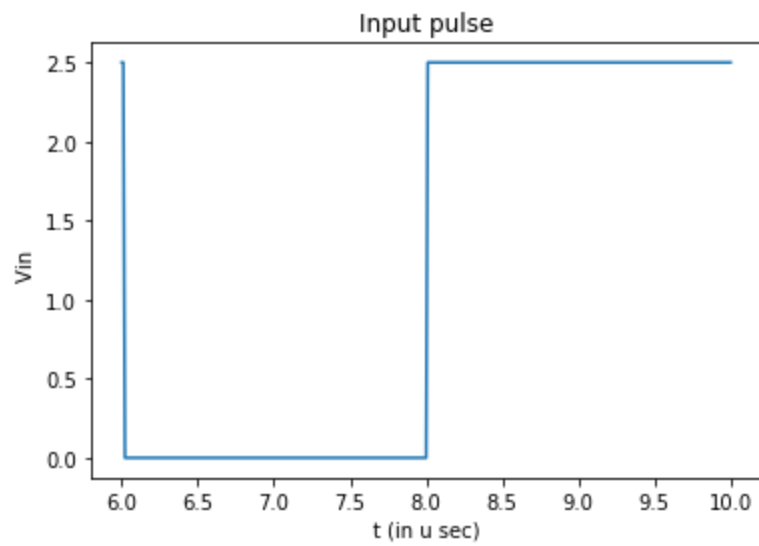wrdata 5.c.1.dat V(input)
wrdata 5.c.2.dat V(vout)
.endc
.end
```



Parameters obtained from the simulation

Parameter	Value
t_r	494.04 ns
t_f	14.37 ns
t_{plh}	154.25 ns
t_{phl}	7.79 ns
t_p	81.07 ns

- **Comment on t_r and t_f ..**

$T_r \gg T_f$, reason being the RC circuit changes when during the transition. For rise time we consider R_L , while for the fall time we consider R_{ON} . Since $R_{ON} < R_L$ here. The capacitor charges and discharges at different rates.

- **Geometric parameters :** The max. Operating frequency for a particular MOSFET depends on t_p (propagation delay), i.e; how fast will it be responding for the switch. T_p inturn depends on the R_{eq} and thus depends on the (W/L) ratio.

- **Max. operating frequency :**

$$f_{max} = 1 / t_p = 1 / (81.07 \text{ ns}) = 12.33 \text{ MHz}$$

- **Dynamic power dissipation :**

$$P_D = C_L * (V_{gs} - V_t) * V_{DD} * f_{max}$$

$$= 0.225 \text{ mW}$$

THE END